

COMPUTER SYSTEMS AND ORGANIZATION

Part 1

Daniel G. Graham Ph.D



ENGINEERING




Contents

1. Transistor Fundamentals
2. Build Gates from transistors
3. Using a breadboard to build a gate
4. Combine Gates to build logic circuits
5. Express logic circuits as equations

SKILLS

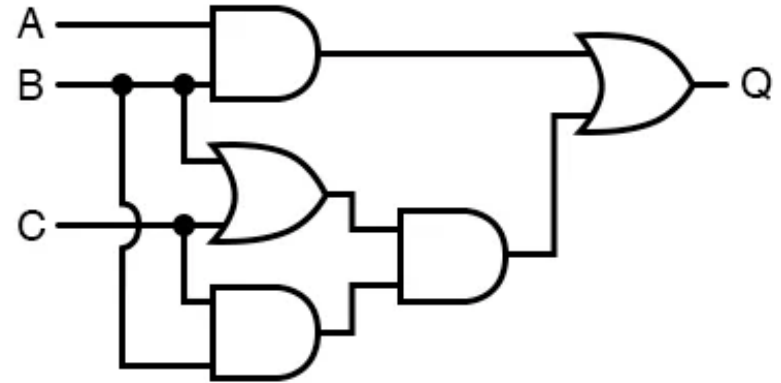1. By the end of this lecture, you should be able to look at the circuit on the right and tell what it will output given different inputs
2. You should be able to express the circuit as a Boolean logic equation
3. Understand how to combine gates to implement a Boolean logic equation.
4. Combine transistors to implement a gate or logic circuit.




RESOURCES

dlbooks.org

Beej's Guide to C Programming

Brian "Beej Jorgensen" Hall

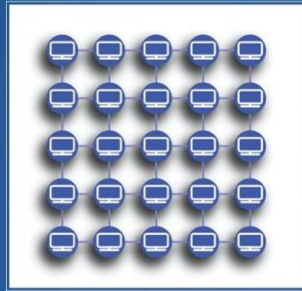Beej's Guide to Network Programming Using Internet Sockets




Brian "Beej Jorgensen" Hall

THIRD EDITION COMPUTER SYSTEMS A PROGRAMMER'S PERSPECTIVE










BRYANT • O'HALLARON

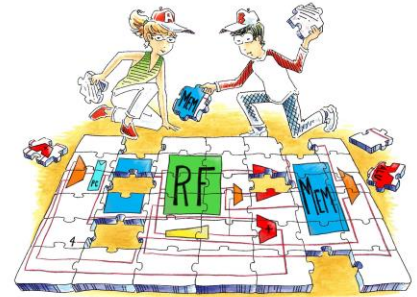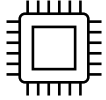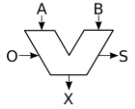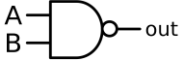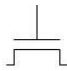Digital Design and Computer Architecture RISC-V Edition



MK
MORGAN KAUFMANN

Sarah L Harris
David Harris

Application Software	
Operating system	
Architecture	
Micro Architecture	
Gates	
Devices	
Physics	

C

Linux

Risc-V

Data path, Stages

Nand, NOR, NOT ..


Field Effect Transistors

Electrons

WHAT ARE LOGIC GATES

- Logic gates are circuits that perform logic functions
 - such as AND, OR, (NOT) , etc
- Logic gates have different symbols and their behavior is normally described using a truth table.

AND

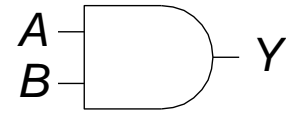


$$Y = AB$$

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

BUILD AN AND GATE FROM SWITCHES

AND

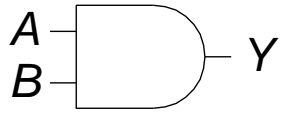


$$Y = AB$$

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

Draw an example

CHALLENGE BUILD AN OR GATE FROM SWITCHES

OR

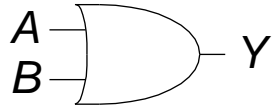


$$Y = A + B$$

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	1
1	0	1
1	1	1

Draw an example

INTRODUCING THE IDEA OF VDD AND GND

AND

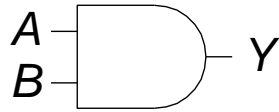

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Draw an example





BUT WE DON'T WANT TO MANUALLY OPEN AND
CLOSE SWITCHES.


OUR END GOAL IS DO
MATH WITH ELECTRICITY

WE NEED A SWITCH THAT WE CAN OPEN AND
CLOSE WITH ELECTRICITY


TRANSISTOR

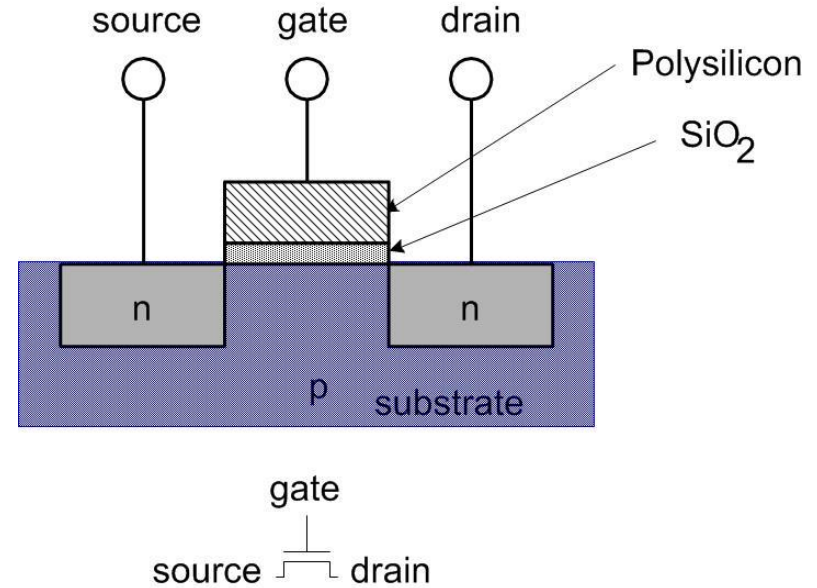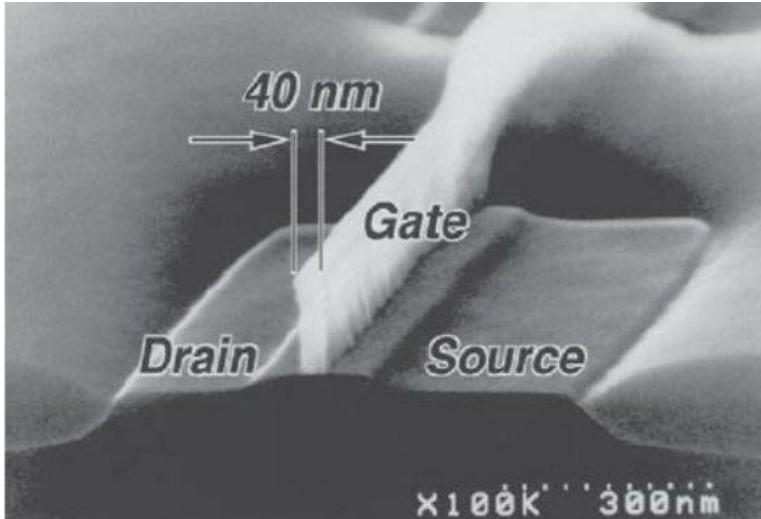

WE'LL FOCUS ON THE BEHAVIOR

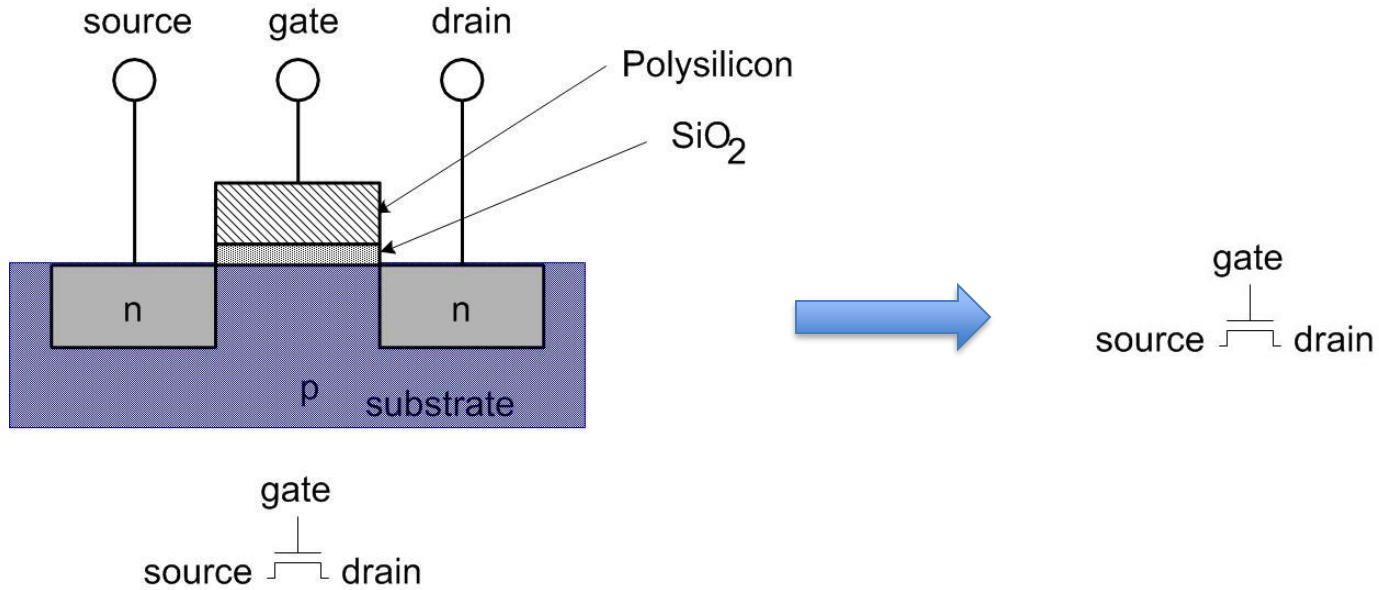

THINKING OF TRANSISTORS AS SWITCHES

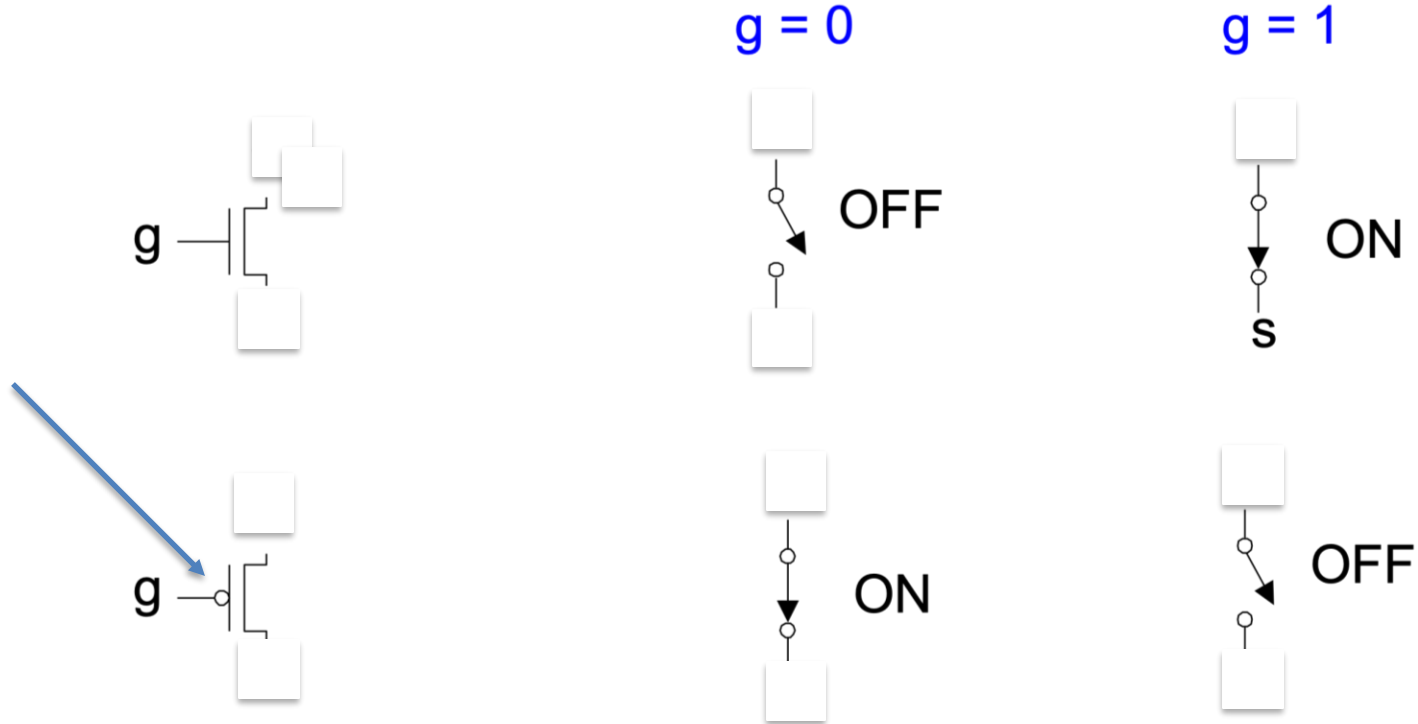

HOW CAN WE COMBINE SWITCHES TO IMPLEMENT LOGIC


CAN WE USE TRANSISTORS TO BUILD GATES

Questions we need to answer

- What are logic gates?
- How do logic gates work?
- Are there different types of gates?

SINGLE INPUT VS TWO INPUT GATES


NOT

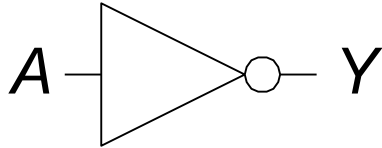

$$Y = \bar{A}$$

A	Y
0	1
1	0

OR

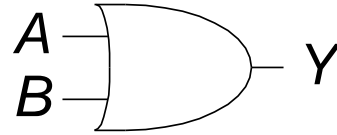


$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


BUILD AN AND GATE FROM TRANSISTORS

THINKING OF TRANSISTORS AS SWITCHES

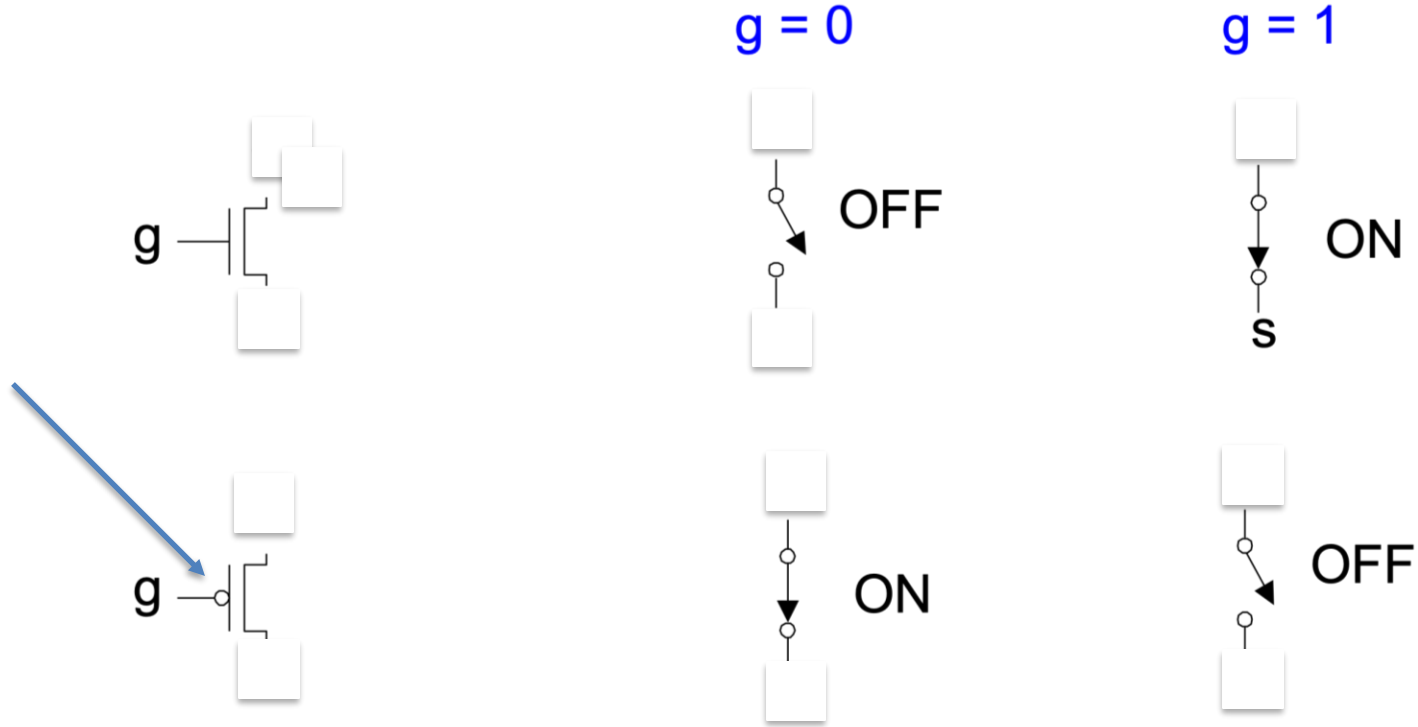


NOT GATE

NOT

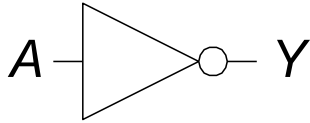

$$Y = \bar{A}$$


A	Y
0	1
1	0

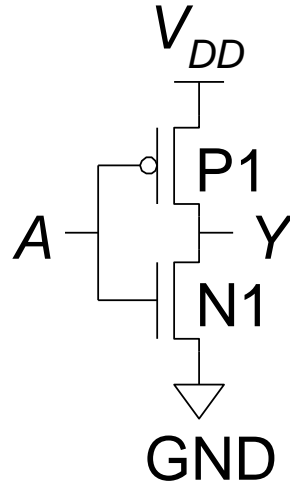

A	P1	N1	Y
0			
1			

MORE LOGIC GATES


XOR

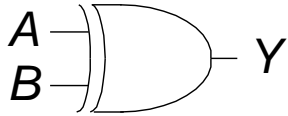

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


NAND

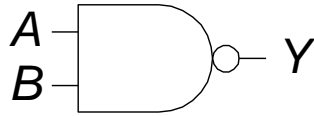

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOR

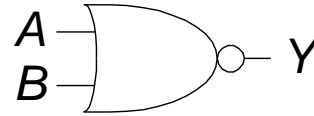

$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


XNOR

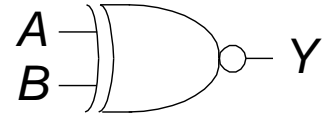

$$Y = \overline{A \oplus B}$$


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


NAND

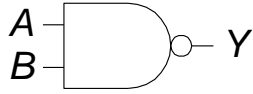

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

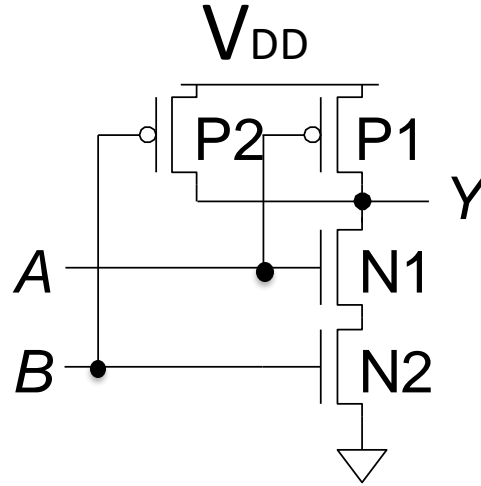


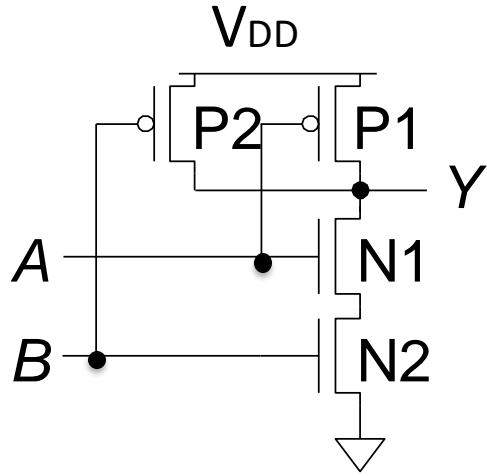


A	B	P1	P2	N1	N2	Y
0	0					
0	1					
1	0					
1	1					

WHAT IS THE OUTPUT OF THIS CIRCUIT?

A	B	C	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

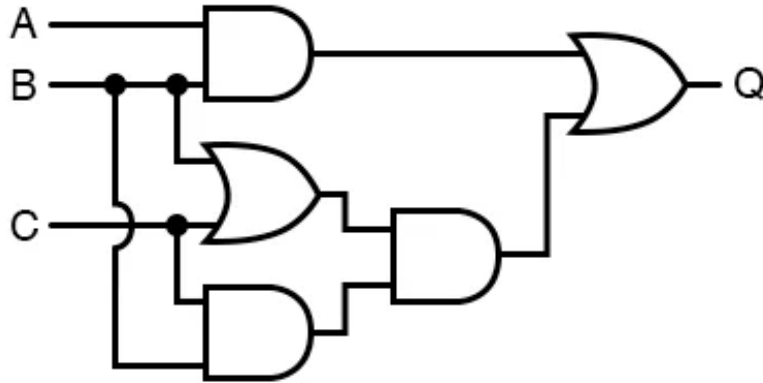


EXPRESS CIRCUIT AS AN EQUATION

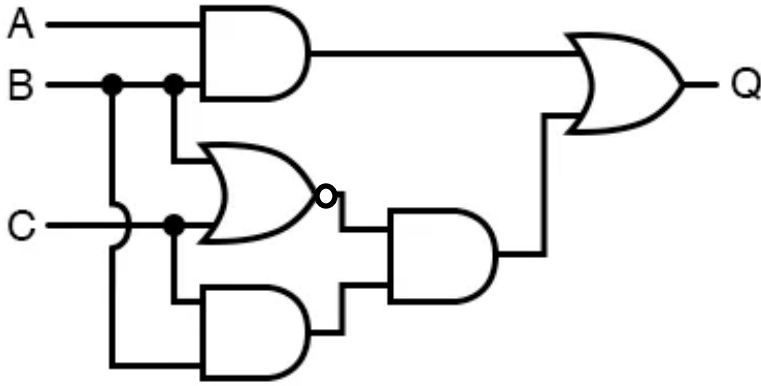

Write the equation representing the circuit. Note I replaced the OR with a NOR.

EXAM QUESTION

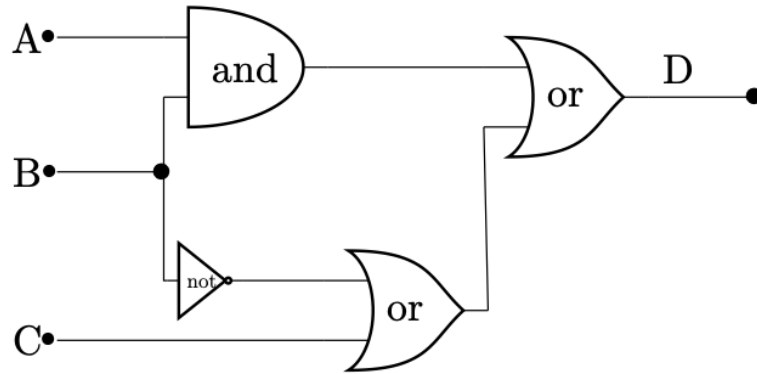

SPRING 2022
Midterm 1

Fill in the following truth table for this circuit:

A	B	C	D
0	0	0	
0	0	1	
0	1	0	
0	1	1	

7. (2 points) Consider the following ~~push-pull~~ network. Which gate does it implement? (Hint: write out the truth table.)

Pull up pull down

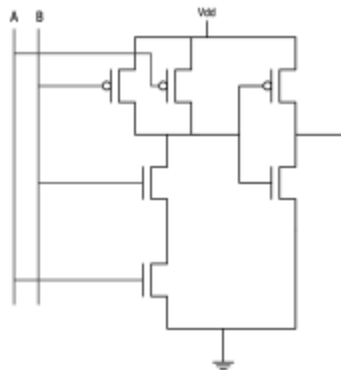


Figure 1: Push-Pull Network, output is the unlabeled wire on the right.

- AND
- OR
- NAND
- XOR
- NOR
- None of the above

CREATIVE QUESTIONS

NAND GATES ARE TURNING COMPLETE

It is possible to implement every other gate by using NAND. You can implement the complete CPU using only NAND gates. What a beautiful building block right 😊


Hint: Start by asking NOT what a NAND gate can do for you but what you can do with a NAND gate.

Use a NAND gate to implement the following gates:


NOT

1. AND
2. OR
3. NOR
4. XOR


NAND Gate Symbol

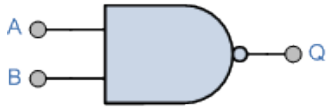


NOT Gate (Inverter)

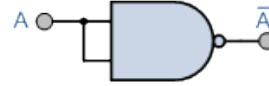


AND Gate

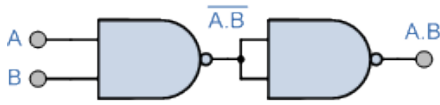


Buffer

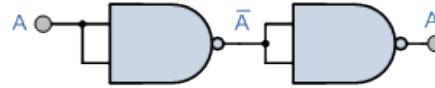


OR Gate

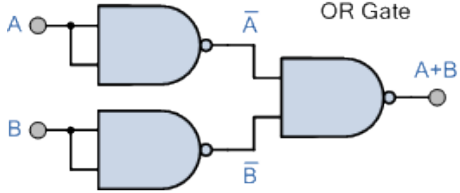

Exclusive-OR

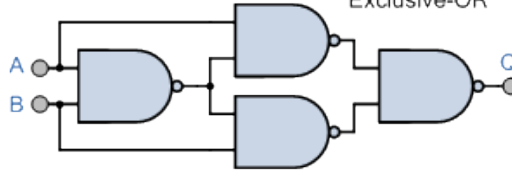

NOR Gate

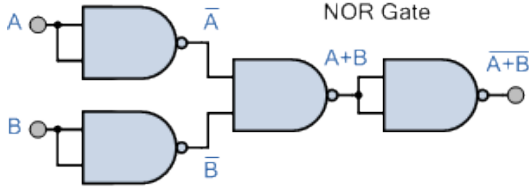

Exclusive-NOR

